

Design of 12-hour Clock in Verilog



Ujwal Vikas Uttarwar (21307R021)

Department of Electrical Engineering
**Indian Institute of Technology
Bombay**

Problem Statement

Design a set of counters suitable for a 12-hour clock system with an AM/PM indicator. These counters will be driven by a high-frequency clock signal (clk) and will be incremented by one every time a pulse is received on the 'ena' input, indicating a one-second interval. A 'reset' input will be used to set the clock to 12:00 AM. The 'pm' signal will be 0 for AM and 1 for PM. The counters include 'hh'

for hours, 'mm' for minutes, and 'ss' for seconds, each represented by two Binary-Coded Decimal (BCD) digits. It's important to note that the reset operation takes precedence over the enable operation and can occur even when the enable signal is not active.

To provide clarity on the operation, consider the following timing diagram which illustrates the transition from 11:59:59 AM to 12:00:00 PM, as well as the behavior of synchronous reset and enable signals.

Verilog Code –

```
module top_module(  
  
    input clk,  
  
    input reset,  
  
    input ena,  
  
    output pm,  
  
    output [7:0] hh,  
  
    output [7:0] mm,  
  
    output [7:0] ss);  
  
    wire ena1,ena2,ena3;  
  
    BCD_SS_MM Sec(clk,reset,ena,ena1,ss);  
  
    BCD_SS_MM Min(clk,reset,ena1,ena2,mm);  
  
    BCD_HH Hr(clk,reset,ena2,ena3,hh);  
  
    AM_PM AP(clk,reset,ena3,pm);  
  
endmodule
```

```

module BCD_SS_MM(

    input clk,

    input reset,

    input ena_in,

    output ena_out,

    output [7:0] q);

    assign ena_out = ena_in&q[3:0]==4'd9&q[7:4]==4'd5;

    always @ (posedge clk)

        begin

            if(reset)

                begin

                    q<=8'd0;

                end

            else if(ena_in&~(q[3:0]==4'd9))

                begin

                    q[3:0]<=q[3:0]+4'd1;

                end

            else if(ena_in&q[3:0]==4'd9&~(q[7:4]==4'd5))

                begin

                    q[3:0]<=4'd0;

                    q[7:4]<=q[7:4]+4'd1;

                end

            else if(ena_in&q[3:0]==4'd9&q[7:4]==4'd5)

```

```
        begin

            q<=8'd0;

        end

    end

endmodule
```

```
module BCD_HH(

    input clk,

    input reset,

    input ena_in,

    output ena_out,

    output [7:0] q);

    assign ena_out = ena_in&q[3:0]==4'd1&q[7:4]==4'd1;

    always @ (posedge clk)

        begin

            if(reset)

                begin

                    q<=8'b00010010;

                end

            else if(ena_in&~(q[3:0]==4'd9)&q[7:4]==4'd0)

                begin

                    q[3:0]<=q[3:0]+4'd1;

                end

            else if(ena_in&q[3:0]==4'd9&q[7:4]==4'd0)
```

```

        begin

            q[3:0]<=4'd0;

            q[7:4]<=q[7:4]+4'd1;

        end

    else if(ena_in&~(q[3:0]==4'd2)&(q[7:4]==4'd1))

        begin

            q[3:0]<=q[3:0]+4'd1;

        end

    else if(ena_in&q[3:0]==4'd2&q[7:4]==4'd1)

        begin

            q<=8'b00000001;

        end

    end

endmodule

```

```

module AM_PM(

    input clk,

    input reset,

    input ena_in,

    output pm);

    always @ (posedge clk)

        begin

            if(reset)

                begin

                    pm<=1'b0;

```

```

        end

        else if(ena_in)

            begin

                pm<=~pm;

            end

        end


    end

endmodule


```

RESULTS


Reset and Count to 10

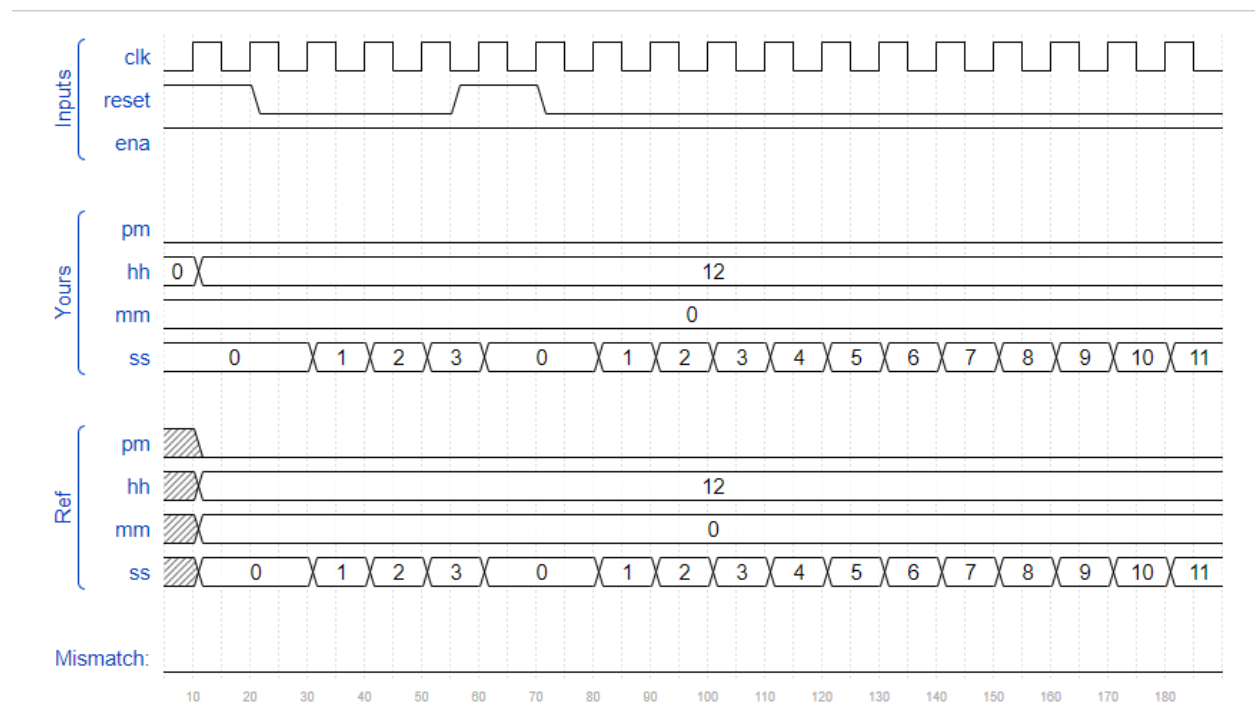

Minute roll-over

 

Hour roll-over

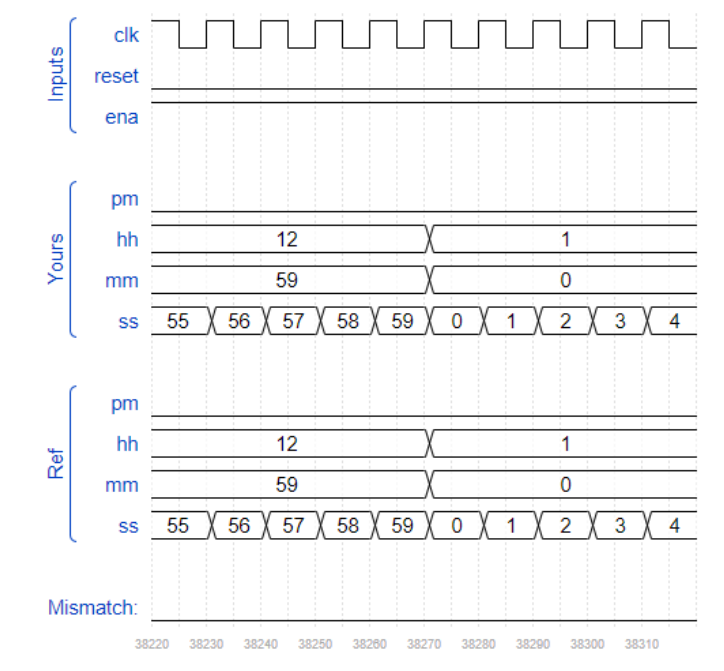

PM roll-over

